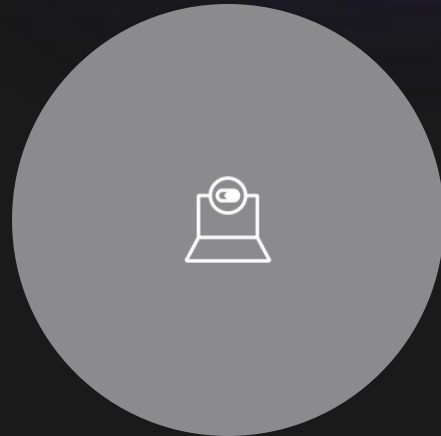




# Pulse-Width Modulation Control of an LED


Zion Joseph de Goes, Cori DeBeatham, Colin Dechambeau


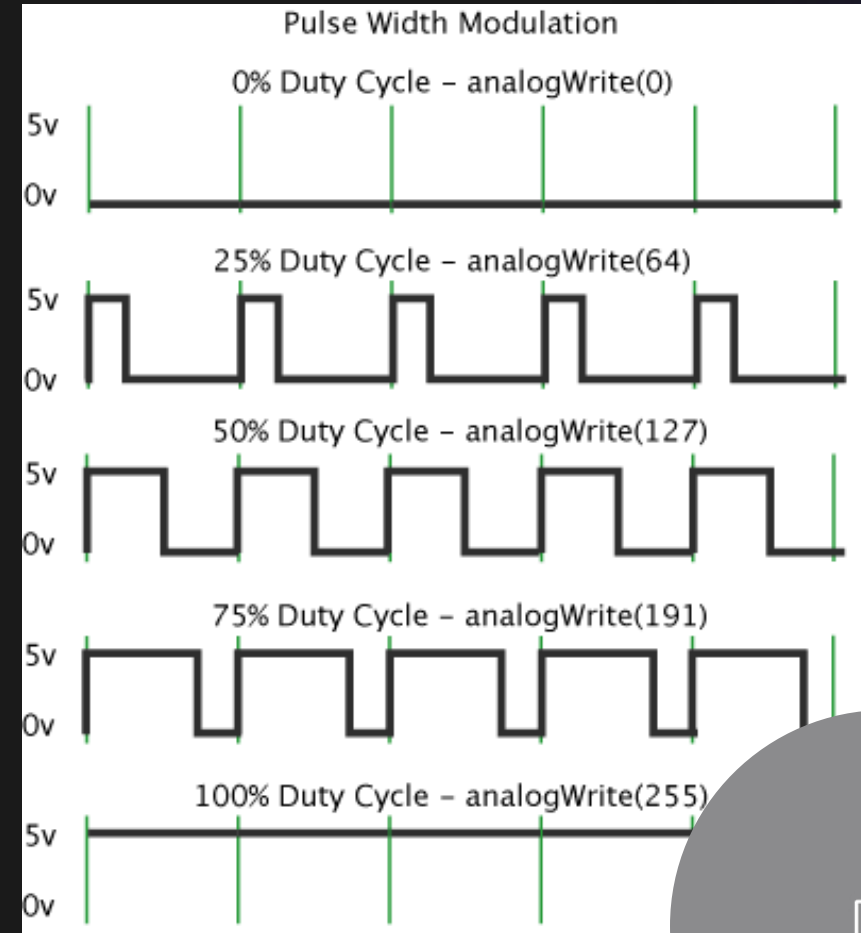
# Goal

Pulse-Width modulation (PWM) is a way to control the voltage to a device through rapid pulses emitting an average voltage rather than a steady voltage. PWM works in duty cycles, where 100% is the maximum voltage and 0% is no voltage.


The goal of this project is to design a system that controls the brightness of an LED via changes in the PWM signal, in response to turning a potentiometer at the input.




Chaitanya Jamboktar, "Pulse Width modulation", 2019.



# Diagram

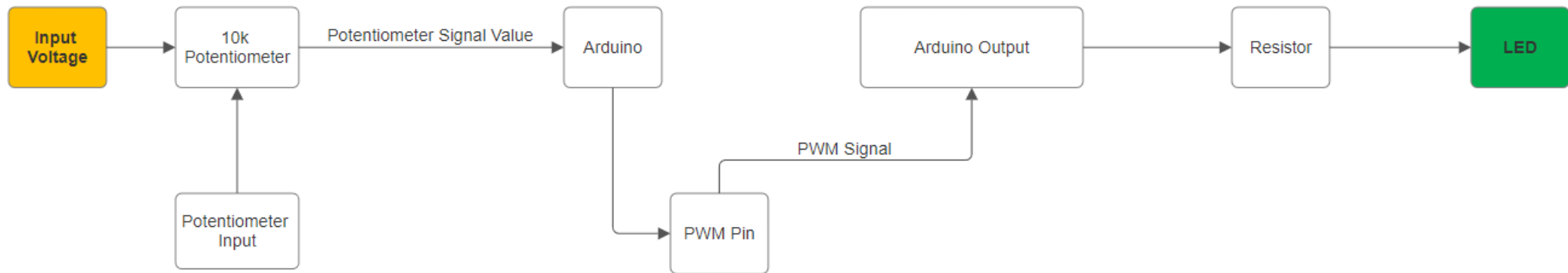

# Mathematical Analysis

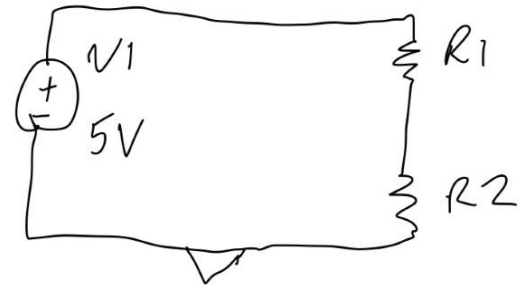

Voltage Divider

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

At half duty R1 and R2 are both at 5k ohms. Using the voltage divider equation  $V_{out} = 2.5V$ . When  $R_2 = 10k$  ohms,  $R_1$  is 0 and  $V_{out} = 5V$ . Finally when  $R_1 = 10k$  ohms,  $R_2$  is 0 and  $V_{out}$  is 0.

$$R_1 = 5K \quad R_2 = 5K$$

$$V_{out} = 5V \left( \frac{5}{5+5} \right) = 2.5V$$

$$R_1 = 0 \quad R_2 = 10K$$


$$V_{out} = 5V \left( \frac{10}{0+10} \right) = 5V$$

$$R_1 = 10K \quad R_2 = 0$$


$$V_{out} = 5V \left( \frac{0}{10+0} \right) = 0$$



# Circuit Simulation

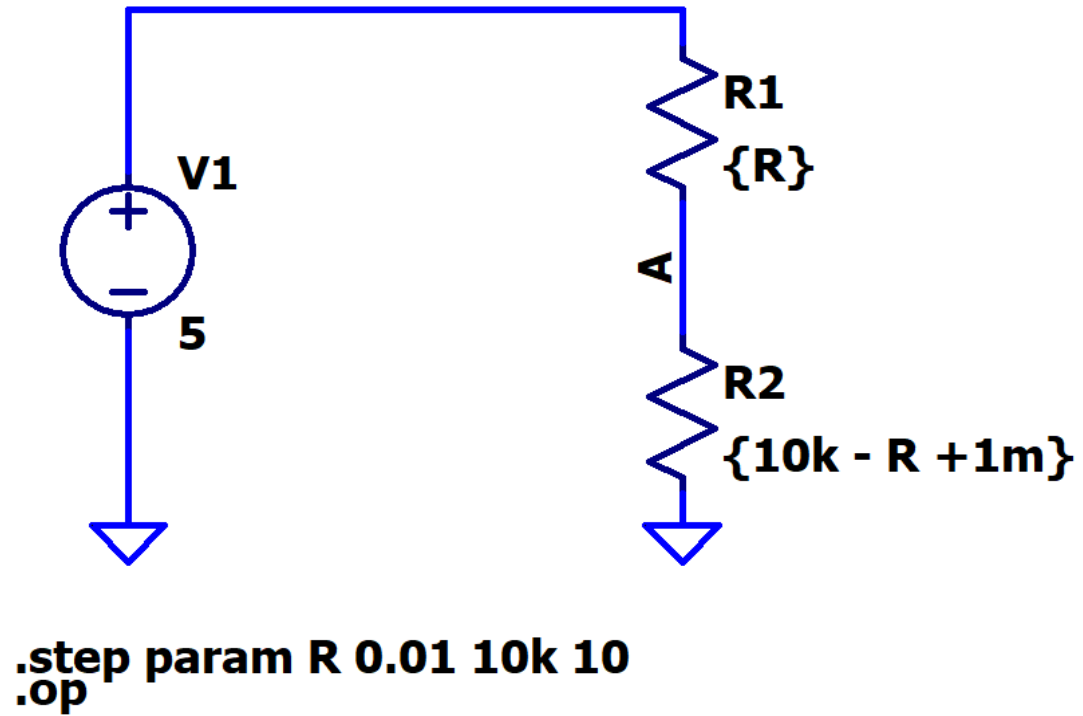


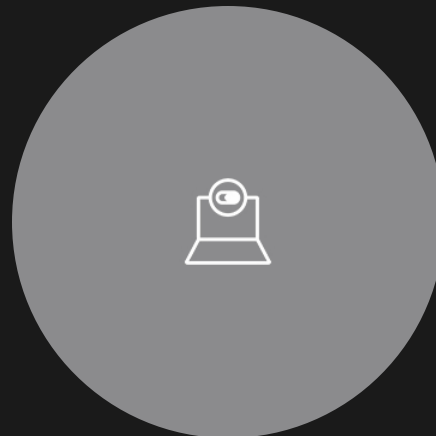Potentiometer Circuit Simulation showing variable resistance






# Circuit Simulation

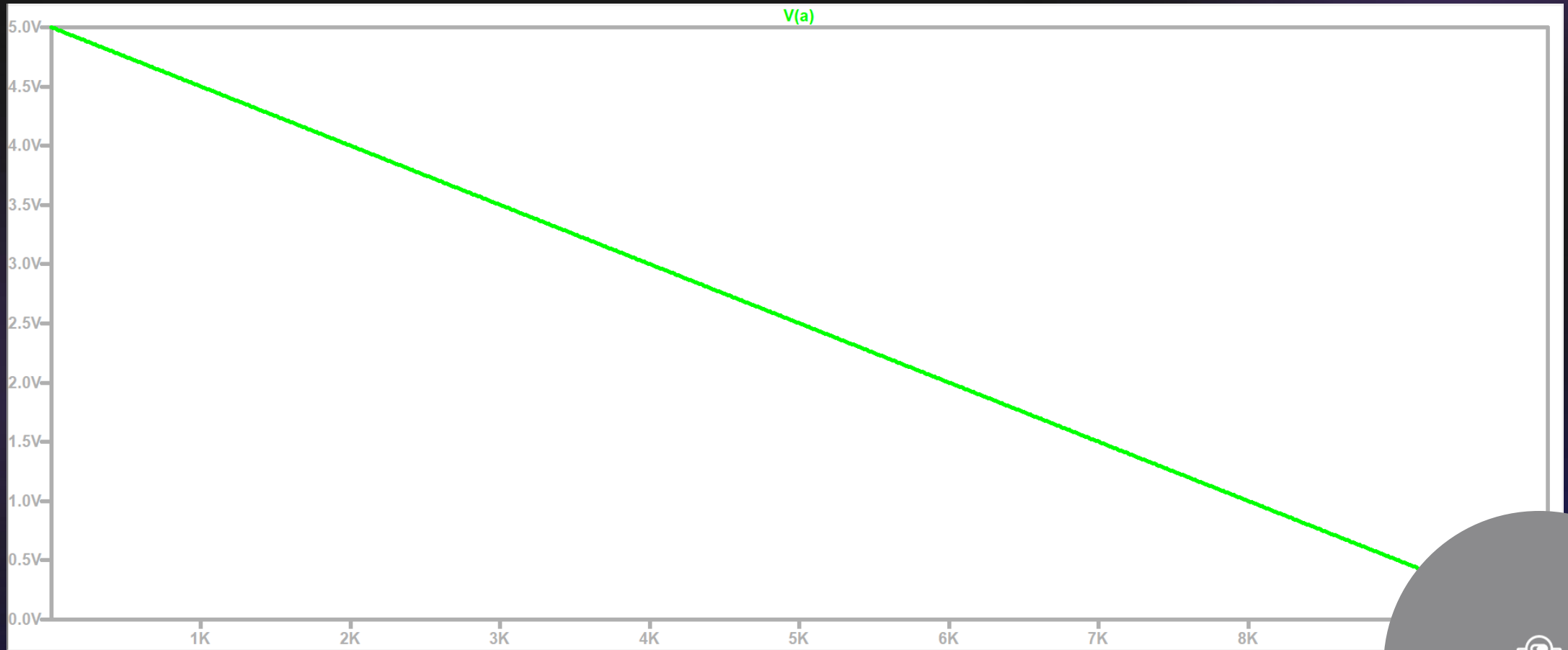

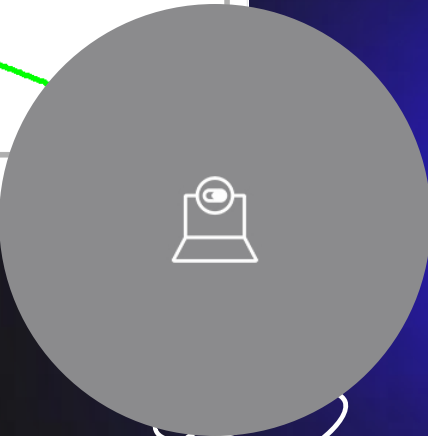**This can be seen as the potentiometer being turned from low resistance to high resistance. Or in other words, the LED being turned from fully on to off.**





# Confirming Our Analysis

## 0% Duty Cycle

**Draft2** [X]

Cursor 1 V(a)

Horz:  Vert:

Cursor 2

Horz:  Vert:

Diff (Cursor2 - Cursor1)

Horz:  Vert:

Slope:

## 50% Duty Cycle

**Draft2** [X]

Cursor 1 V(a)

Horz:  Vert:

Cursor 2

Horz:  Vert:

Diff (Cursor2 - Cursor1)

Horz:  Vert:

Slope:

## 100% Duty Cycle

**Draft2** [X]

Cursor 1 V(a)

Horz:  Vert:


Cursor 2

Horz:  Vert:



Diff (Cursor2 - Cursor1)

Horz:  Vert:

Slope:

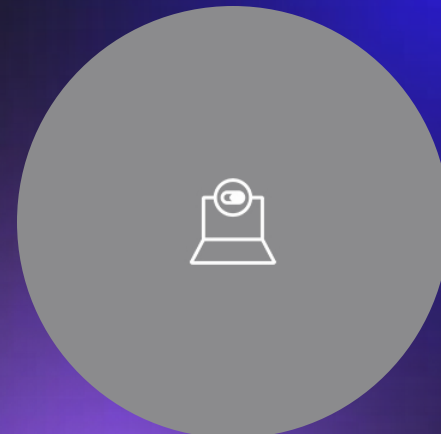

# Our Circuit

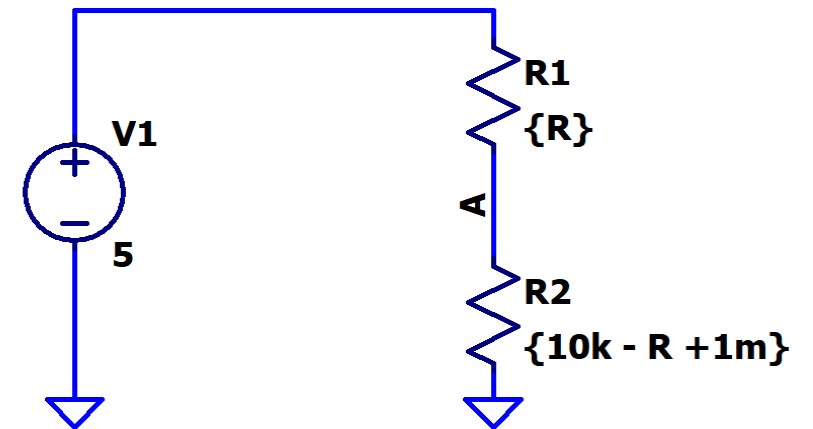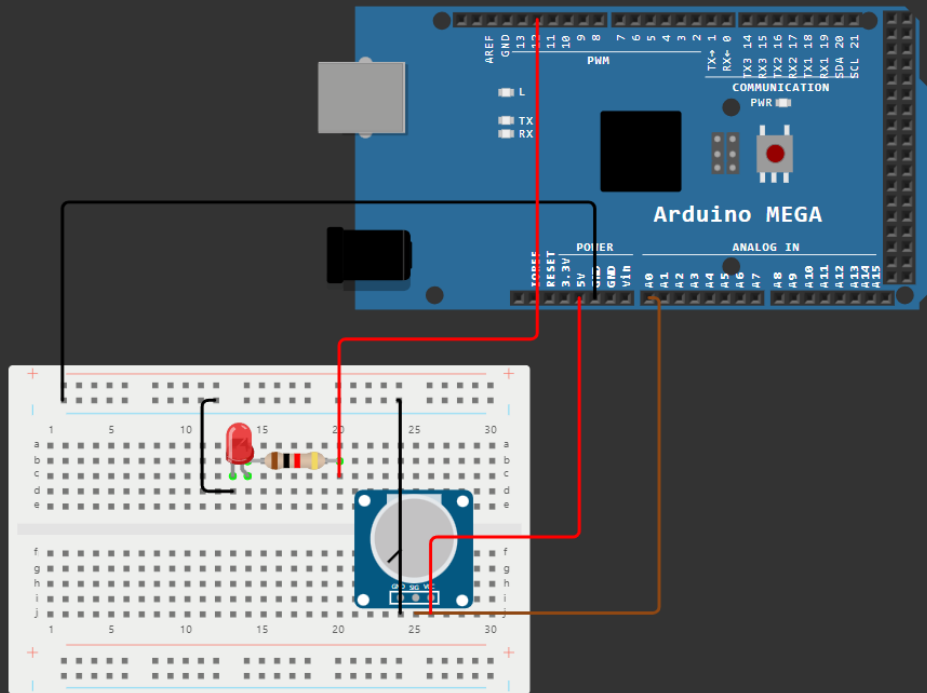

.step param R 0.01 10k 10  
.op






# Arduino Code

PWM\_POT.ino

```
1  const int potPin = A0; // Analog input pin for the potentiometer
2  const int pwmPin = 13; // PWM output pin
3
4  void setup() {
5      pinMode(pwmPin, OUTPUT); // Set the PWM pin as an output
6      Serial.begin(9600); //Start serial monitor
7  }
8
9  void loop() {
10     int potValue = analogRead(potPin); // Read the potentiometer value (originally 0-1023)
11     potValue /= 4; //Squish the value to fit within 0-255
12     analogWrite(pwmPin, potValue); //Set the PWM duty cycle
13
14     Serial.print("Potentiometer Value: ");
15     Serial.println(potValue); //Print Potentiometer Value (works)
16
17 }
```





# Our Circuit

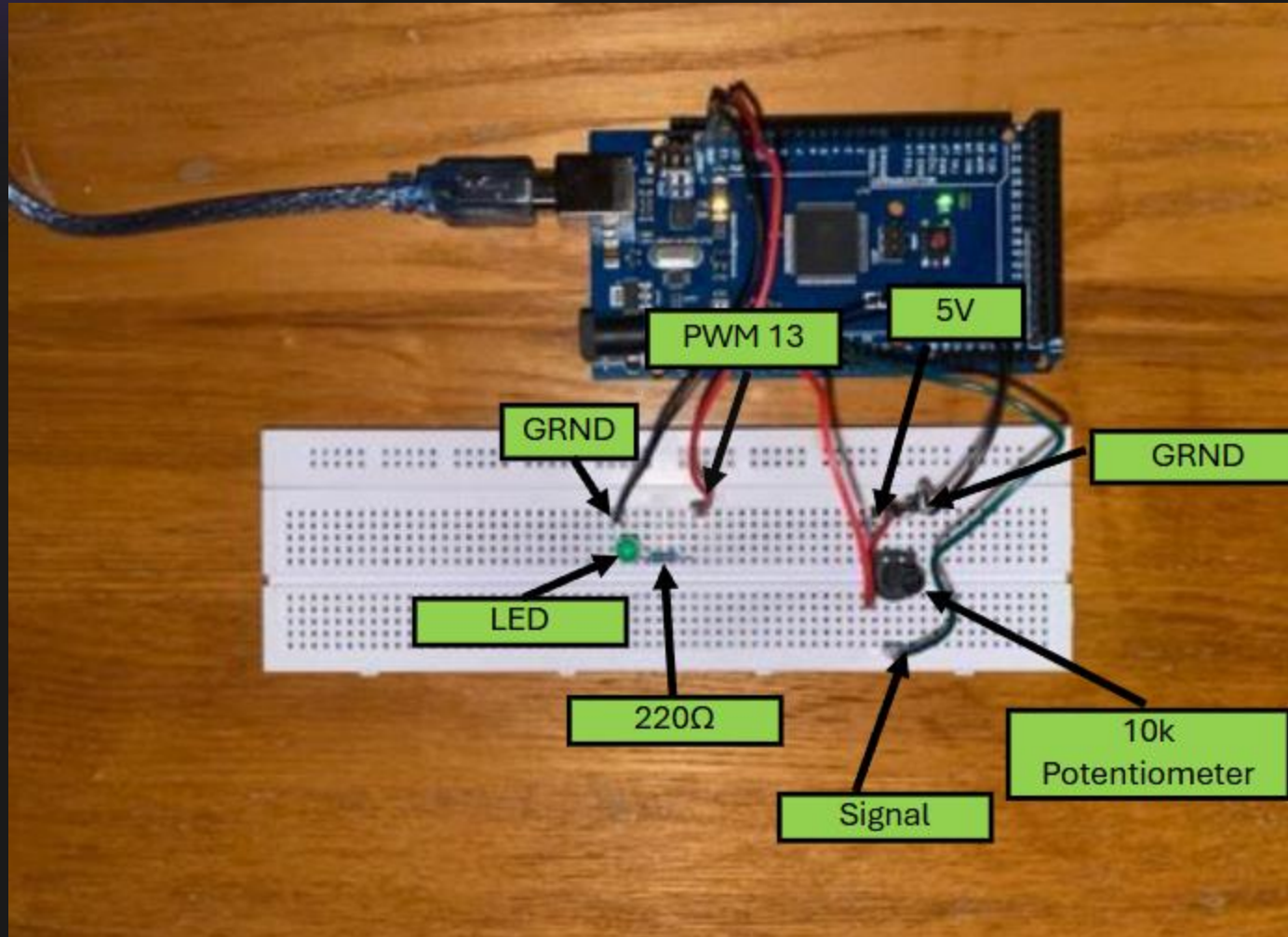



# Experimental Measurement

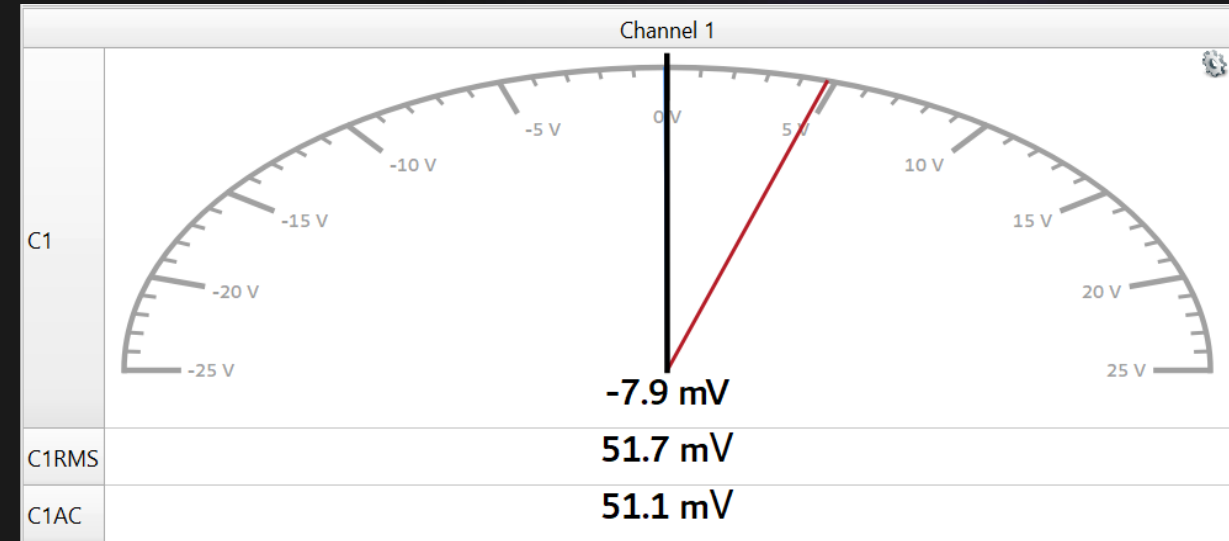
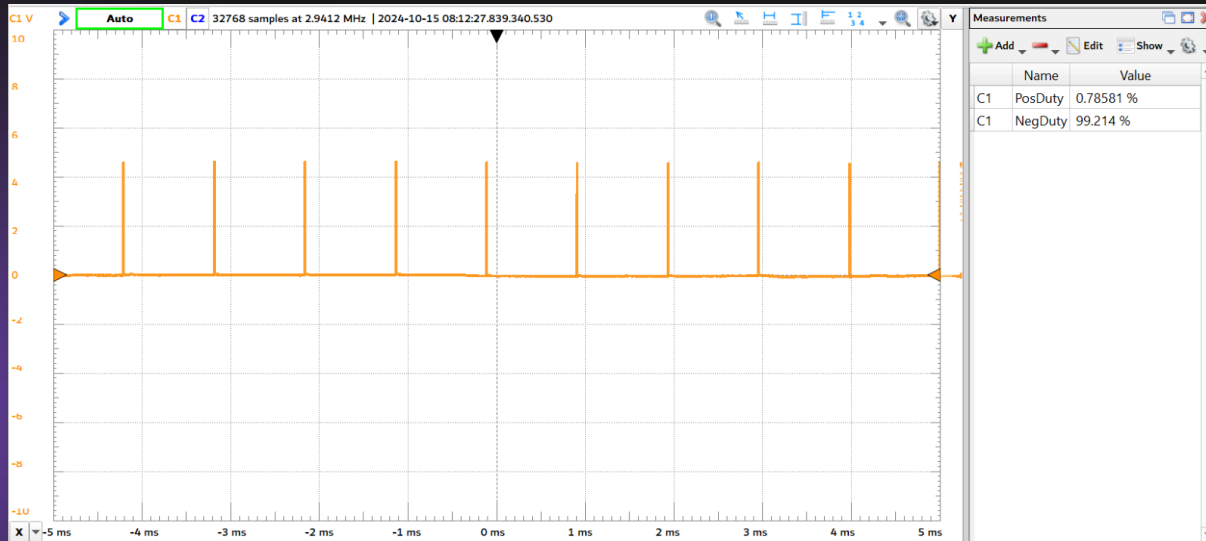


**0% Duty Cycle**  
**(Fits within analysis expectations)**





# Experimental Measurement

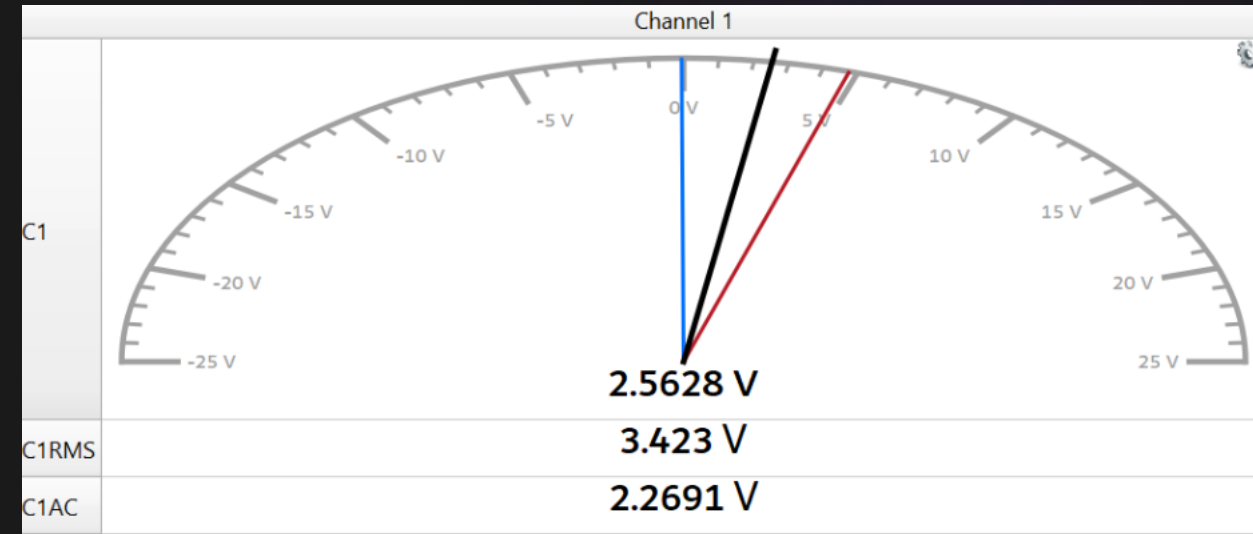
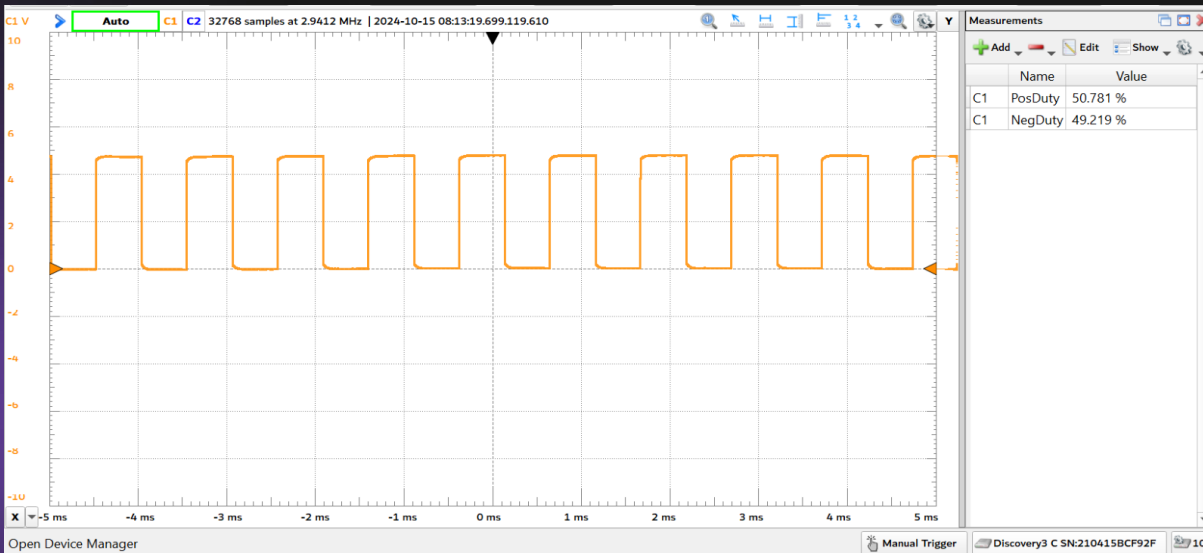


**50% Duty Cycle**  
**(Fits within analysis expectations)**






# Experimental Measurement

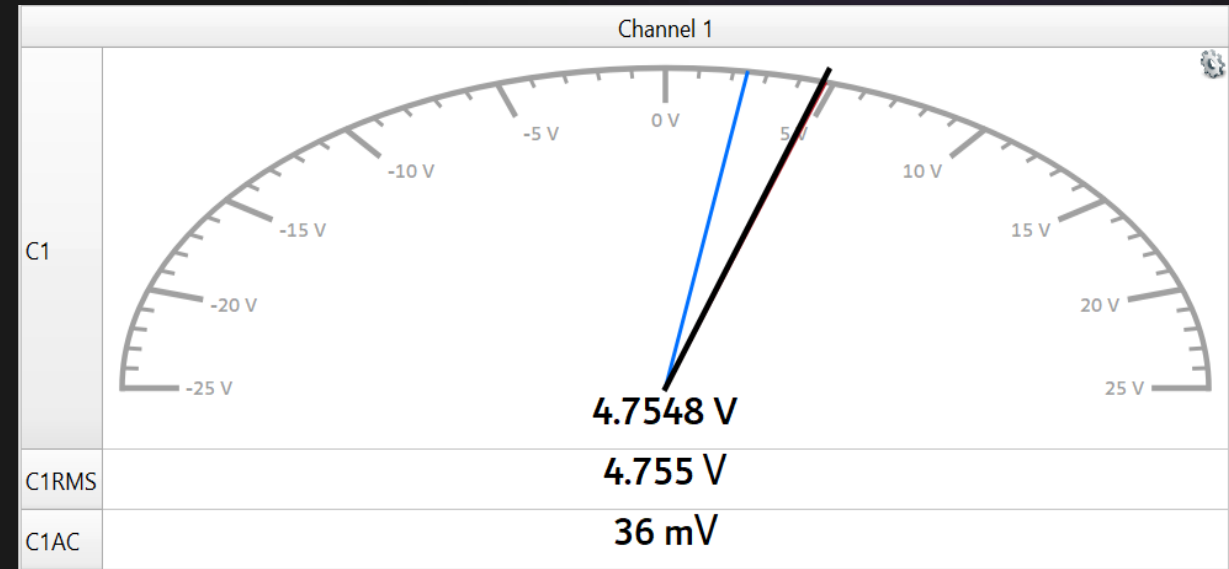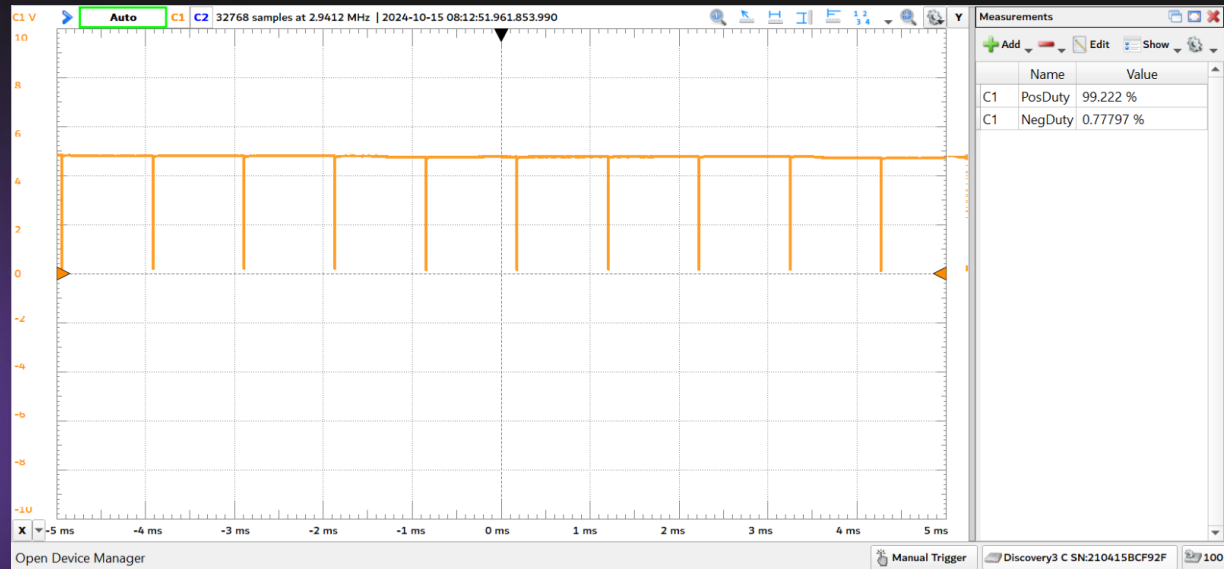

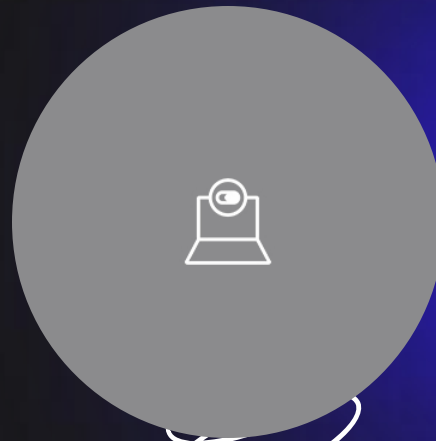**100% Duty Cycle**  
**(Fits within analysis expectations)**









# Design Choices


## 555 Timer

### Advantages:

- Versatile, wide ranges of applications
- Lower power consumption than an entire microcontroller.
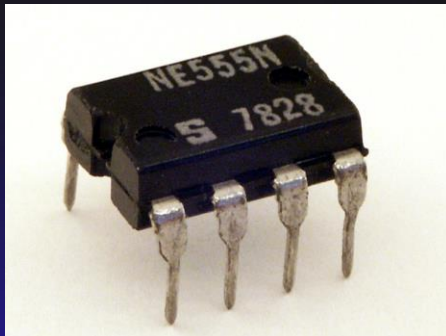
### Disadvantages:

- Higher complexity pinout (needs more wires)
- Not programmable
- Only one PWM output
- Limited by internal tolerances




## Arduino

### Advantages:

- Multi-use for very complex projects.
- Can be programmed in C++
- Multiple PWM outputs
- Very precise
- Serial monitor for real time PWM monitoring.
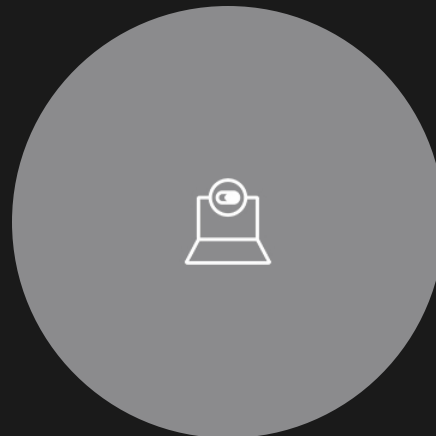
### Disadvantages

- Uses more power
- Bulky to carry around






# New Knowledge

## Microcontrollers

- We used an Arduino as the heart of our project, and PWM is one of its many powers. Many functions of microcontrollers are unknown to us. How are they different from microprocessors anyway? We can learn more in ECSE 4790 - Microprocessor Systems
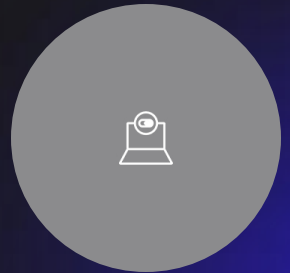
## FFT --> Fast Fourier Transform

- PWM waves are square wave pulses. At its core, these waves can be broken into its components by the FFT. This is something we learned through our research.
- Although we did not have to break down the waves ourselves, we can learn more in ECSE 4530 - Digital Signal Processing.







# Real World Applications



Servo motors are a motor type that use PWM to control the position of the motor. PWM control is efficient and accurate and correlates the duty cycle to the angle of the motor.



## Motor Control (PWM)

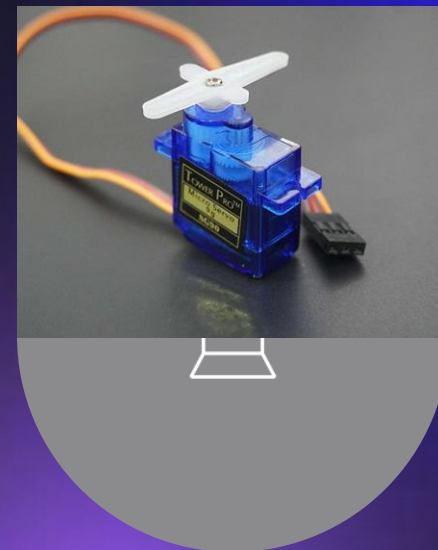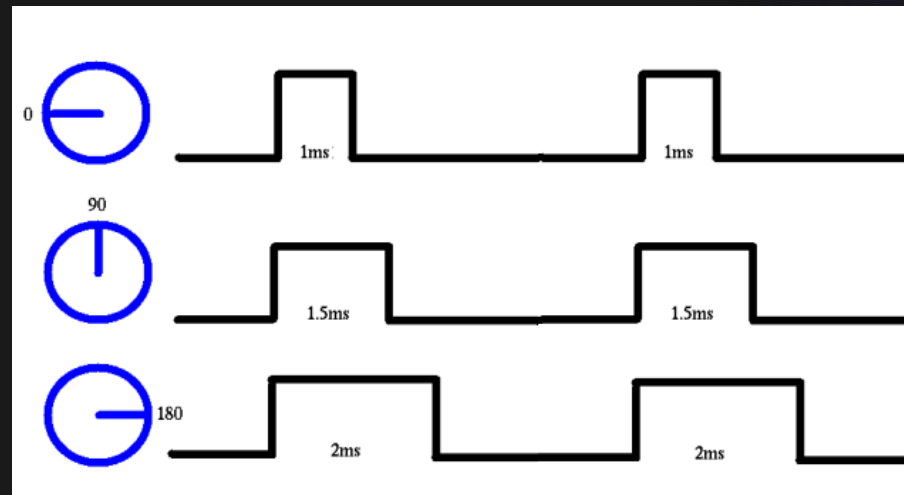



## A Question for you!

- What changes would one have to make to substitute a 555 timer in place of the Arduino, would it change the other components?

